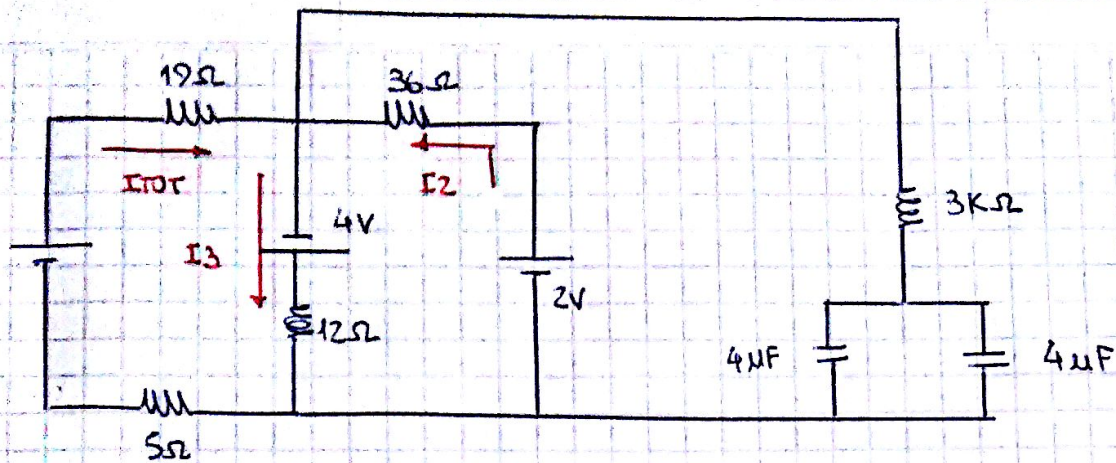




estado estacionario $\rightarrow$ I por $3k\Omega$ es 0
debido a los capacitores

$$P_{R_{19\Omega}} = 0,76W \quad \rightarrow \quad I_{TOTAL} = \sqrt{\frac{P_{R_{19\Omega}}}{R_{19}}} = 0,2A$$

$$(E1) \quad I_{TOTAL} + I_2 = I_3$$

$$(E2) \quad 4V - 12 \cdot I_3 + 2V - 36 \cdot I_2$$

$$\text{de } E1) \quad [I = I_3 - 0,2A]$$

$$\text{en } E2) \quad 4V - 12 I_3 + 2V - 36 (I_3 - 0,2) = 0$$

$$6V - 12 I_3 - 36 I_3 + 7,2V = 0$$

$$13,2V = 48 I_3$$

$$[I_3 = 0,275A]$$

$$[P_{R_{12\Omega}} = I_3^2 \cdot R_{12\Omega} = 0,9075W]$$